

EC_Week 11, Non-assessed

A series LCR circuit with $L = 10 \text{ mH}$, $C = 2 \text{ }\mu\text{F}$ and $R = 5 \text{ }\Omega$ is driven by a generator with an amplitude of 100 V and variable angular frequency ω . Find

(a) the resonant frequency ω_0 and

(b) the rms current at resonance.

When ω is 8000 rad/s find (c) the impedance Z ,

(d) the rms current.