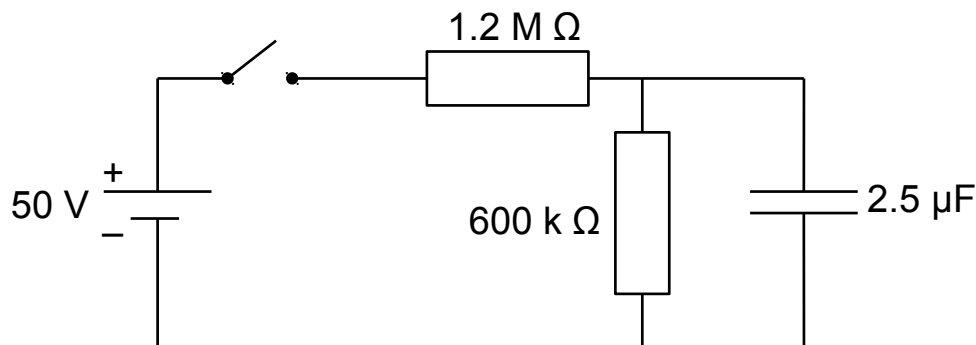


## Electric circuits

### Non-assessed Problem Sheet 5, Solution

1. In the circuit shown below:

- (a) What is the initial battery current immediately after the switch is closed?
  - (b) What is the battery current a long time after the switch is closed?
  - (c) What is the maximum voltage across the capacitor?
  - (d) If the switch has been closed for a long time and is then opened, deduce an expression for the current through the  $600\text{ k}\Omega$  resistor as a function of time.
  - (e) What is the energy dissipated in the  $600\text{ k}\Omega$  resistor after the switch is opened?
- (Note that  $1\text{ k}\Omega = 10^3\text{ }\Omega$ ;  $1\text{ M}\Omega = 10^6\text{ }\Omega$ ;  $1\text{ }\mu\text{F} = 10^{-6}\text{ F}$ .)



## Solution

1. (a) Initially, the capacitor acts like a short-circuit, bypassing the  $600\text{ k}\Omega$  resistor.

$$I = V/R = 50\text{ V} / 1.2\text{ M}\Omega = 41.7\text{ }\mu\text{A}$$

- (b) A long time after the switch is closed, the capacitor is fully charged and acts like an open-circuit.

$$I = V/R = 50\text{ V} / (1.2 + 0.6)\text{ M}\Omega = 50\text{ V} / 1.8\text{ M}\Omega = 27.8\text{ }\mu\text{A}$$

- (c) At this stage, the potential difference across the capacitor is

$$50\text{ V} \times 0.6/1.8 = 16.7\text{ V, by the potential divider rule.}$$

- (d) Total response = Final Value + (Initial Value – Final Value)  $e^{-t/\tau}$

The final value of the current will be zero, as the capacitor is discharging. The total response is therefore,  $I = I_0 e^{-t/RC}$ , where  $I_0 = V/R = 16.7\text{ V} / 600\text{ k}\Omega = 27.8\text{ }\mu\text{A}$  and  $\tau = RC = 1.5\text{ s}$ .

- (e) The energy dissipated is equal to the energy stored in the capacitor.

$$E = \frac{1}{2} CV^2 = 0.5 (2.5 \times 10^{-6} \times (16.7)^2) = 3.5 \times 10^{-4}\text{ Joules.}$$