
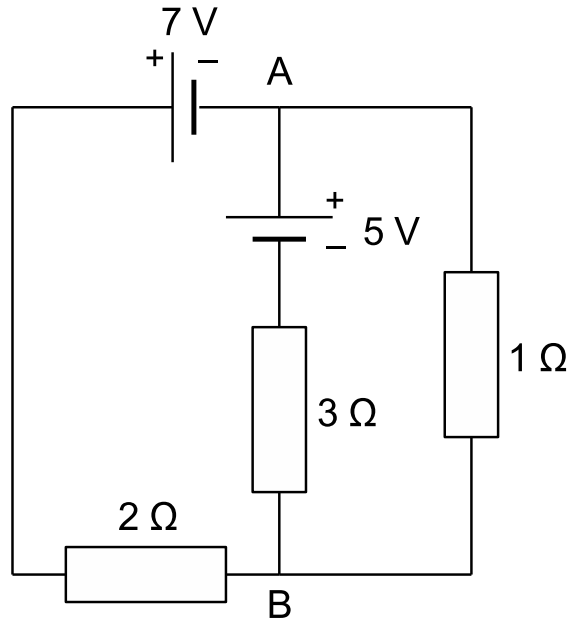


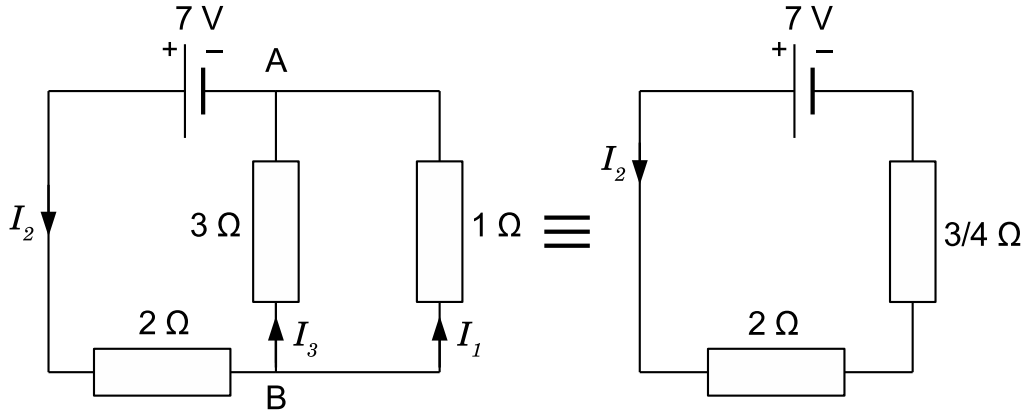Q3: Use circuit shown below and the superposition theorem.



A3 (i) Consider the 7 V source.




Current through the 2 Ω resistor: $I_2 = \frac{V}{R} = \frac{7}{2 + \frac{1}{\frac{1}{3} + 1}} = \frac{7}{\frac{11}{4}} = \frac{28}{11} \text{ A} \rightarrow$. [1]

Current through the 3 Ω resistor: $I_3 = \frac{28}{11} \times \frac{1}{4} = \frac{7}{11} \text{ A} \uparrow$ (using the current splitter rule). [1]

Current through the 1 Ω resistor: $I_1 = \frac{28}{11} - \frac{7}{11} = \frac{21}{11} \text{ A} \uparrow$. [1]

Consider the 5 V source.

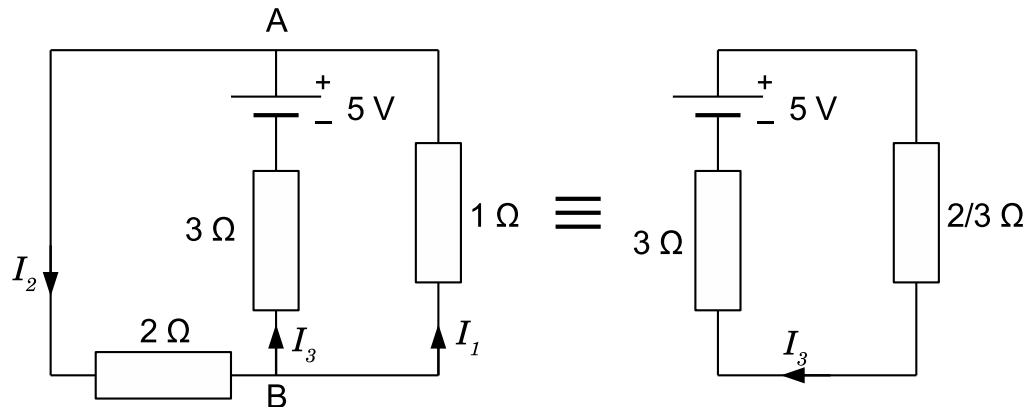

Current through the $3\ \Omega$ resistor: $I_3 = \frac{V}{R} = \frac{5}{3 + \frac{1}{\frac{1}{2} + 1}} = \frac{5}{\frac{11}{3}} = \frac{15}{11}\text{ A} \uparrow$ [1]

Current through the $2\ \Omega$ resistor: $I_2 = \frac{15}{11} \times \frac{1}{3} = \frac{5}{11}\text{ A} \rightarrow$. (current splitter) [1]

Current through the $1\ \Omega$ resistor: $I_1 = \frac{15}{11} - \frac{5}{11} = \frac{10}{11}\text{ A} \downarrow$. [1]

\therefore by superposition,

$$I_2 = \frac{28}{11} + \frac{5}{11} = \frac{33}{11} = 3\text{ A}.$$

$$I_3 = \frac{7}{11} \uparrow + \frac{15}{11} \uparrow = \frac{22}{11} \uparrow = 2\text{ A} \uparrow.$$

$$I_1 = \frac{21}{11} \uparrow + \frac{10}{11} \downarrow = \frac{11}{11} \uparrow = 1\text{ A} \uparrow. \quad [1]$$

(ii) Potential between points A and B. Going from B to A $= -I_3 R + 5V = (-2)(3) + 5V = -1\text{ V}$. [1]

(iii) Power supplied by each battery:

7V: $I_2 * 7 = 3 * 7 = 21\text{ W}$; 5V: $I_3 * 5 = 2 * 5 = 10\text{ W}$. [2]