

Electric circuits

Non-assessed Problem Sheet Week 5, Capacitors

1. In the circuit shown below:

- (a) What is the initial battery current immediately after the switch is closed?
 - (b) What is the battery current a long time after the switch is closed?
 - (c) What is the maximum voltage across the capacitor?
 - (d) If the switch has been closed for a long time and is then opened, deduce an expression for the current through the $600\text{ k}\Omega$ resistor as a function of time.
 - (e) What is the energy dissipated in the $600\text{ k}\Omega$ resistor after the switch is opened?
- (Note that $1\text{ k}\Omega = 10^3\text{ }\Omega$; $1\text{ M}\Omega = 10^6\text{ }\Omega$; $1\text{ }\mu\text{F} = 10^{-6}\text{ F}$.)

