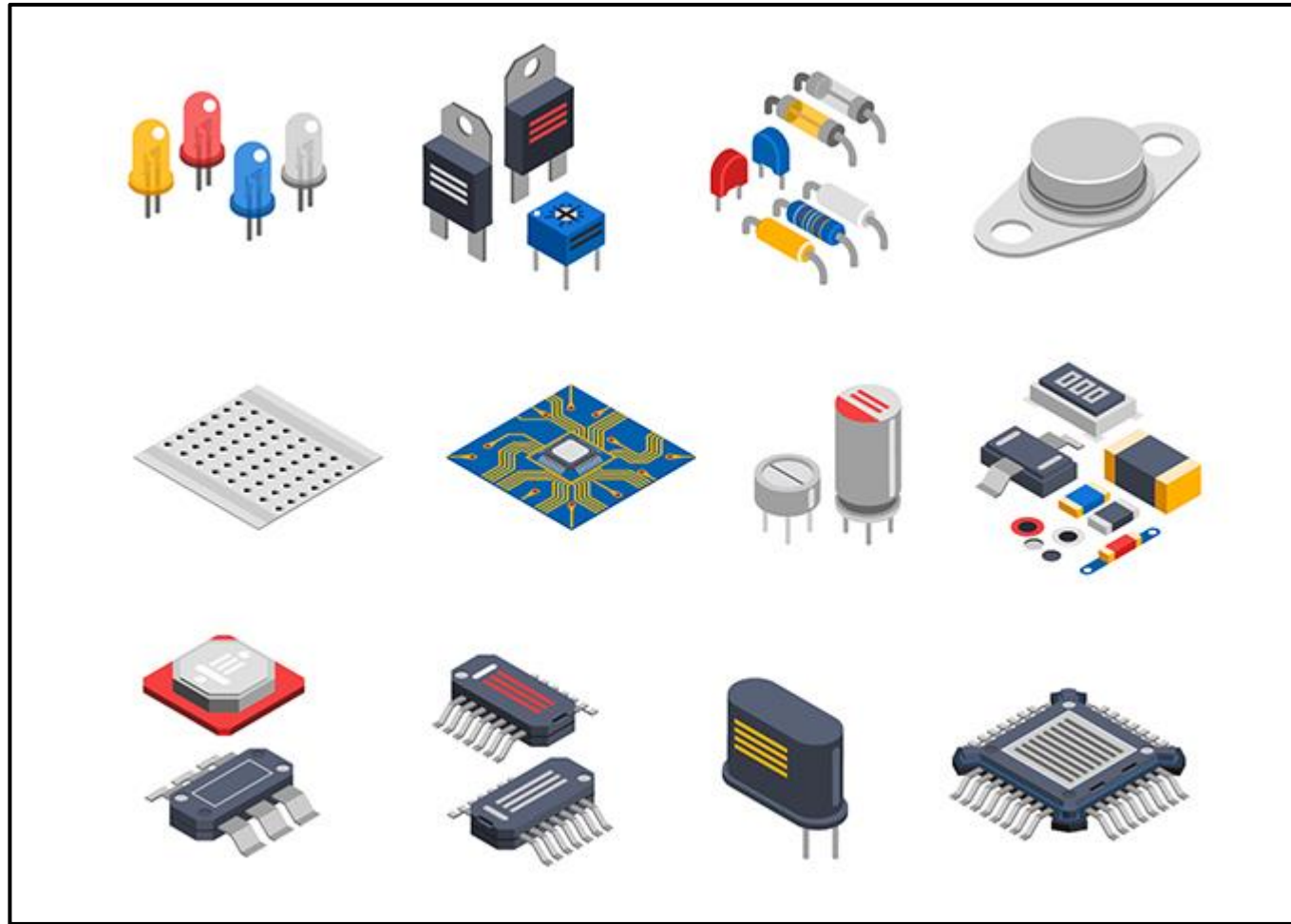


ELECTRIC CIRCUITS



Vera Guarrera - v.guarrera@bham.ac.uk

Week 01 Materials: Electric Circu

+

← → ↺ 🏠

🔒 🔑 ⚙️ https://canvas.bham.ac.uk/courses/65833/pages/week-01-materials?module_item_id=28 ⭐

🔍 Search

📌

⬇️

📄

👤²

ABP

📌

☰

⋮

Electric Circuits > Pages > Week 01 Materials

👤 Student view

📖 Immersive Reader

2022/23

Home

Modules

Announcements 🔗

Assignments

Discussions

Grades

People

Quizzes 🔗

Panopto

Zoom

Pages 🔗

Collaborations 🔗

BigBlueButton 🔗

Syllabus 🔗

Outcomes 🔗

Files 🔗

Rubrics

View all pages

✔️ Published

✎ Edit

⋮

Week 01 Materials

Week 01 lecture slides:

Week 01 typed notes: [01_Lecture_notes.pdf](#) ⬇️

The Panopto recording of this weeks lecture can be seen **HERE**

Non-assessed problem sheets for this week:

[ec_na_week1_q.pdf](#) ⬇️ and [ec_na_week1_b.pdf](#) ⬇️

Solutions

[ec_na_week1_a-1.pdf](#) ⬇️ , [ec_na_week1_b_a-1.pdf](#) ⬇️

◀ Previous

Next ▶

👤

Account

🛡️

Admin

🕒

Dashboard

📖

Courses

📅

Calendar

📧¹²

Inbox

🕒

History

↺

Commons

🍷

PebblePa
d


♿


Accessibil



Photonic quantum computer: **Jiuzhang** (2020)



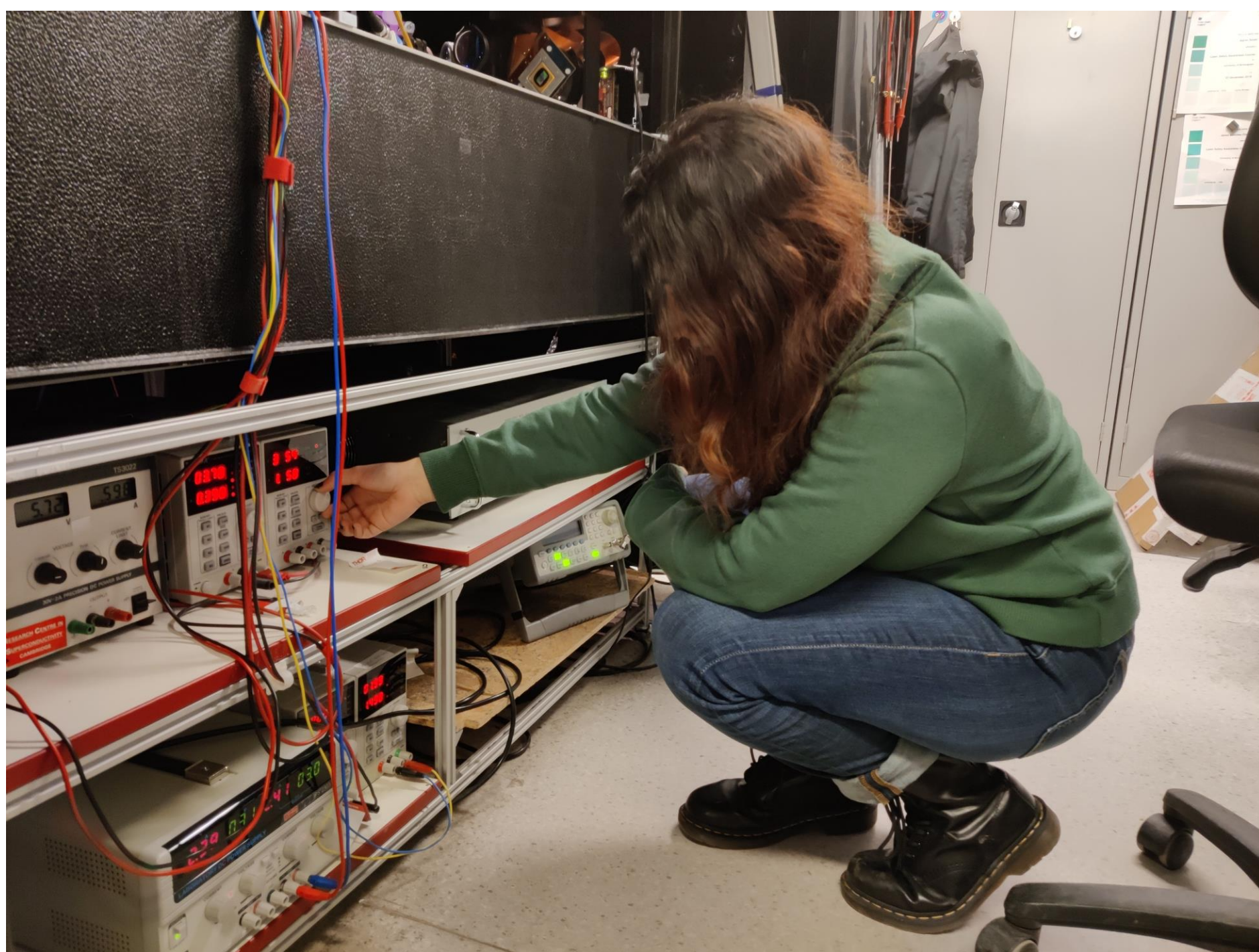Phd student Symran
working in the
Quantum Systems group



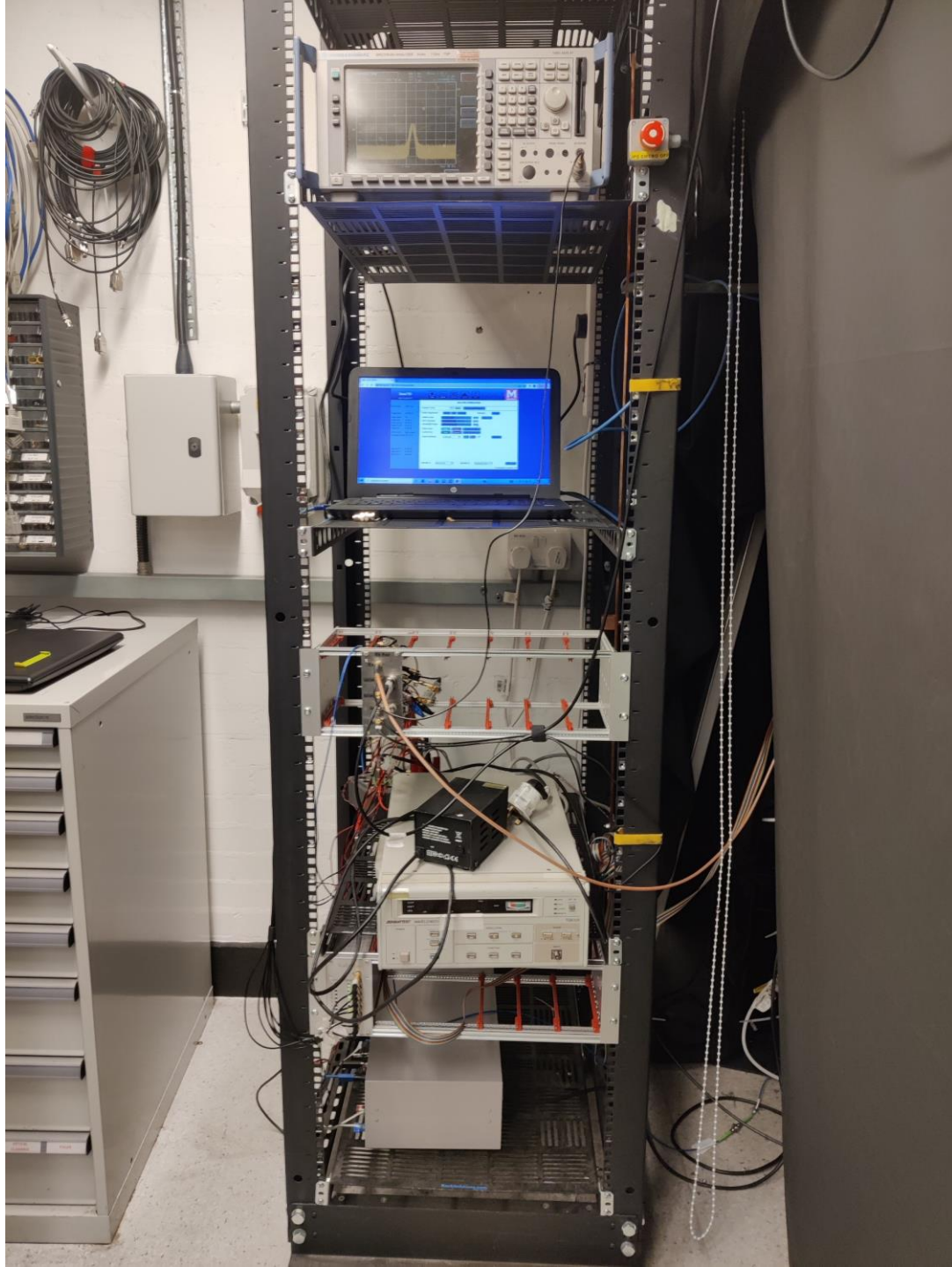

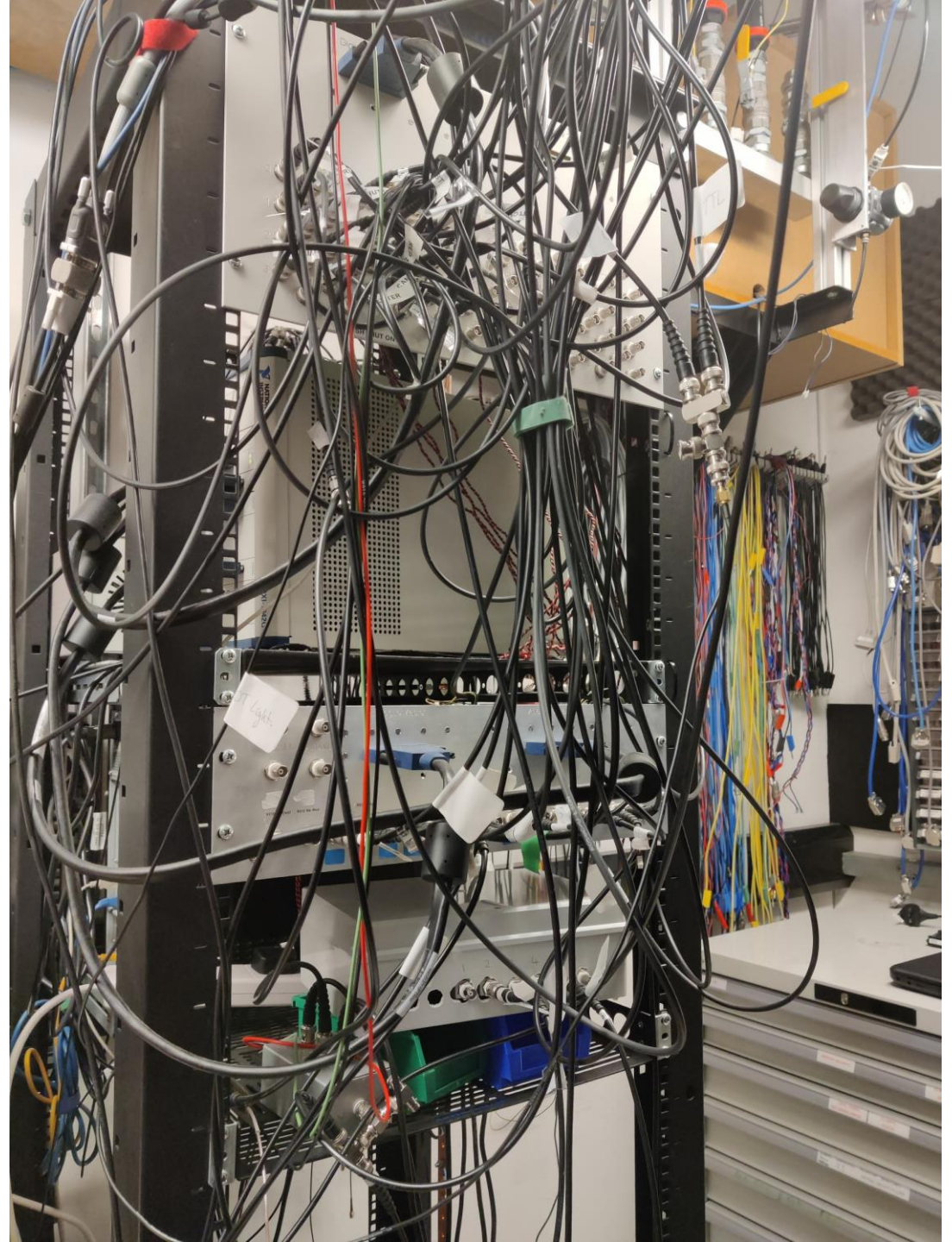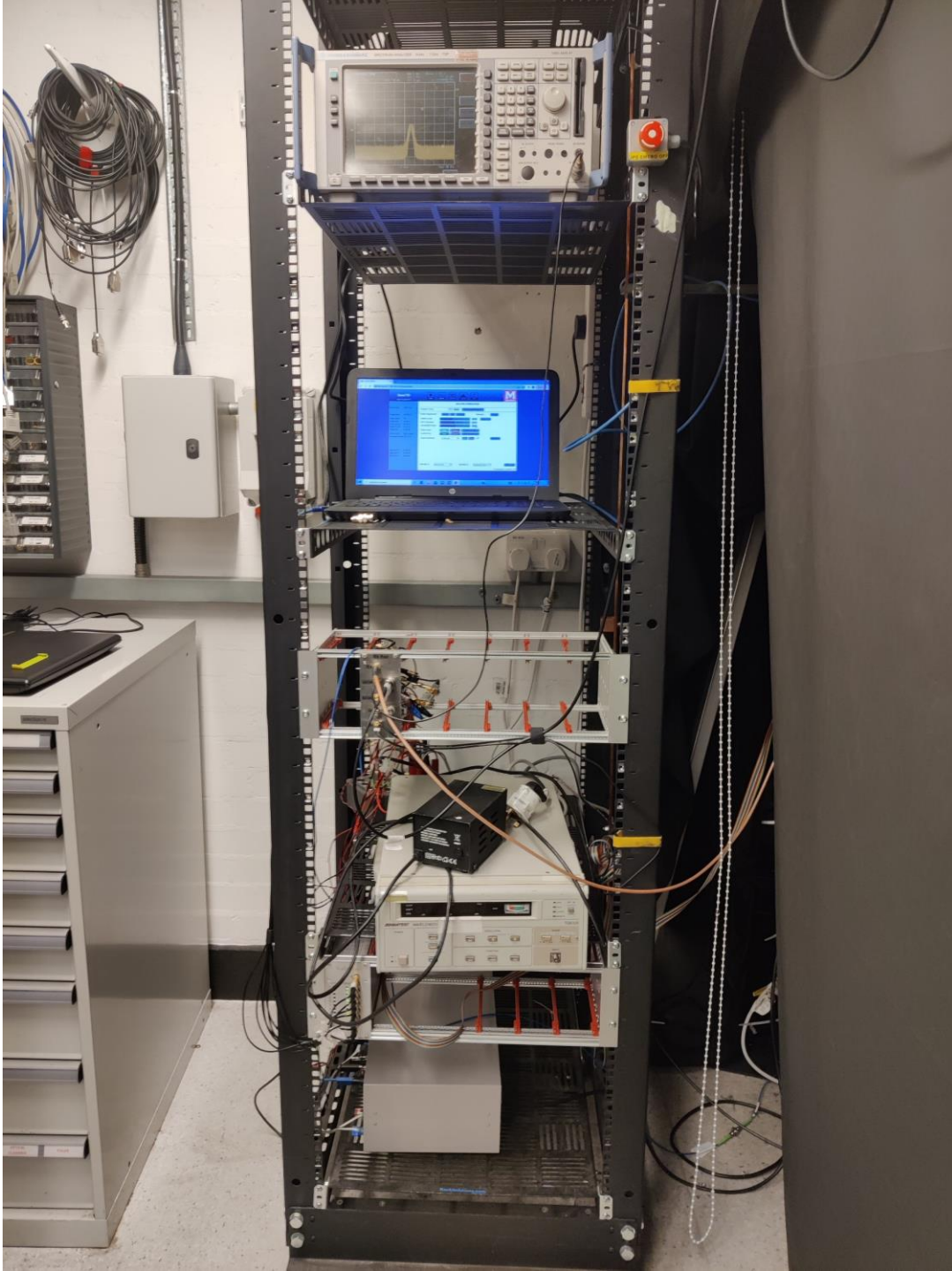

Recommended textbooks

- **University Physics**

Young and Freedman

Suggestions for further reading will be given at the end of each lecture

- **Introduction to Electric Circuits**

Ray Powell. Highly recommended! Main Library - short loan, (5 copies)

- **Physics for scientists and engineers (5th edition)**

Paul A. Tipler and Gene Mosca

- **Electric Circuits (TK3226)**

P. Silvester. School of Electrical Engineering Library, (9 copies)

- **Introductory Circuit Theory (TK3226)**

J.K.Fidler and L. Ibbotson. Main Library - short loan, (2 copies)

- **The art of Electronics – *For advanced reading***

P. Horowitz and W. Hill

Syllabus

- **Direct current (DC) circuit analysis** (4 sessions)
Current, voltage, Ohm's law, Kirchhoff's law, Thevenin's theorem, Superposition theorem
- **Transient response** (2 sessions)
Capacitors, inductors, RC and RL circuits, response to pulses
- **Alternating current (AC)**
- **Circuit analysis** (4 sessions)
Phasors, complex impedance, RC and RL filters, LCR circuits, resonance, and Q factor.

Week 01: material covered

Units and definitions: current, voltage, power


Resistance, Ohm's law

Dimensional analysis

Resistors in series and in parallel

Voltage divider and current splitter


Practical applications

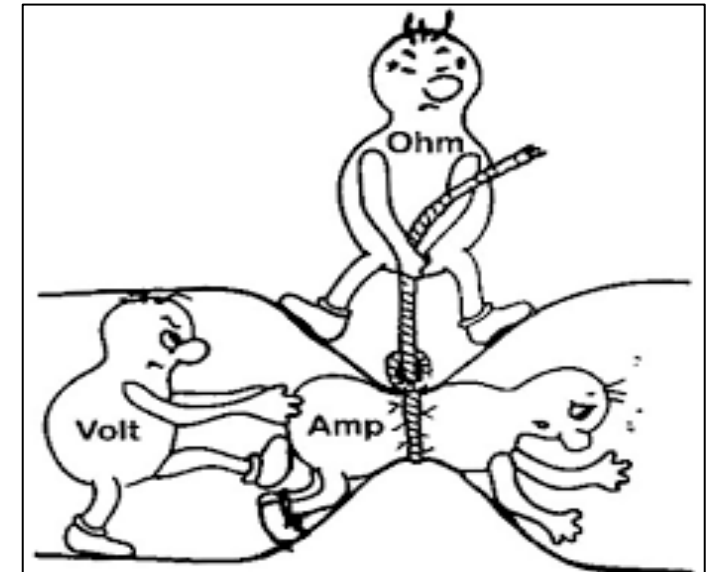

Definition

What is an Electrical Circuit?

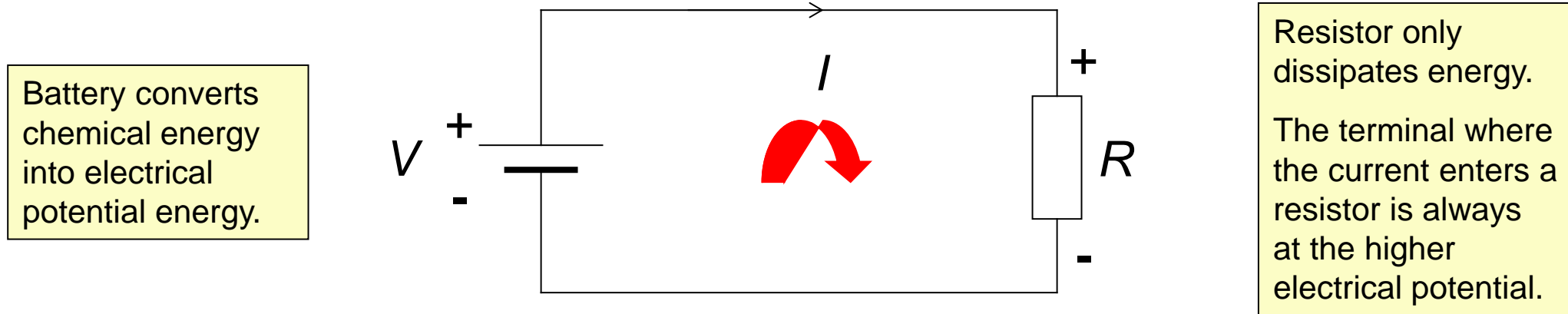A closed path around which an electrical current may flow.



- Contains one or more **active** devices which deliver energy.
e.g. battery - or a source of Electromotive Force (EMF)
- Contains **passive** devices (e.g. resistors) which dissipate energy.
- Current is taken to flow from points of higher electrical potential to points of lower electrical potential.
- Conventional current flow is **opposite** to that of electrons.

Units

- **Charge (Coulomb, C)**

The unit of electrical charge is the Coulomb. Charge is quantized, that is, it comes in discrete amounts. The charge of an electron is -1.602×10^{-19} C.

- **Current (Ampere, A)**

Electric current is defined as the rate at which charge flows through a given point in a circuit: $I = \frac{\Delta Q}{\Delta t}$

- **Potential Difference (Volt, V)**

The work done when transferring charge from one point in a circuit to another: $V = \frac{\Delta W}{\Delta Q}$


- **Resistance (Ohm, Ω), Ohm's law**

The ratio of the voltage across a circuit element to the current flowing through it.

- **Power (Watt, W) is defined as the rate of doing work.**

Resistance and Ohm's law



- I-V characteristics

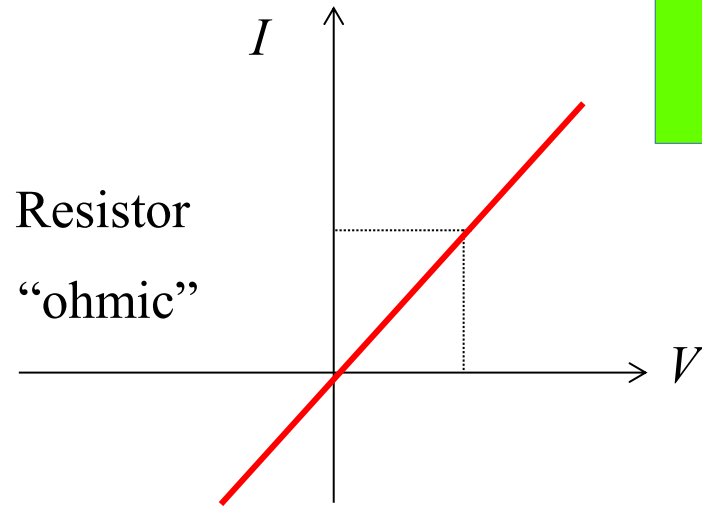



$$I = \frac{V}{R}$$

Dynamic resistance


$$r = \frac{dV}{dI}$$

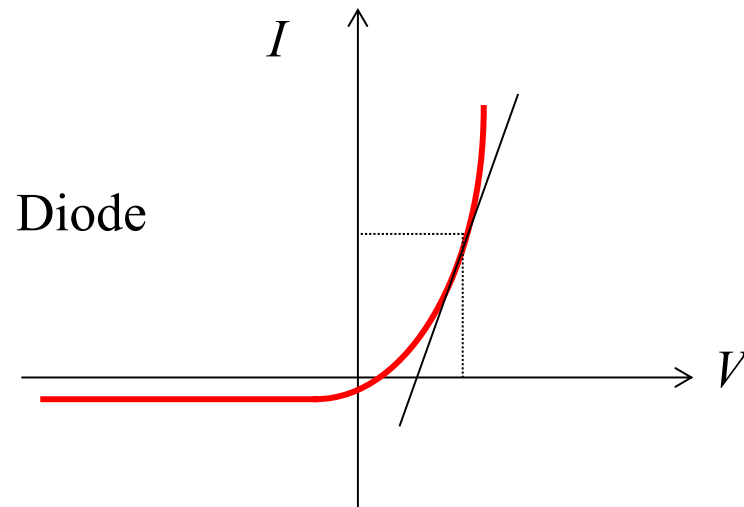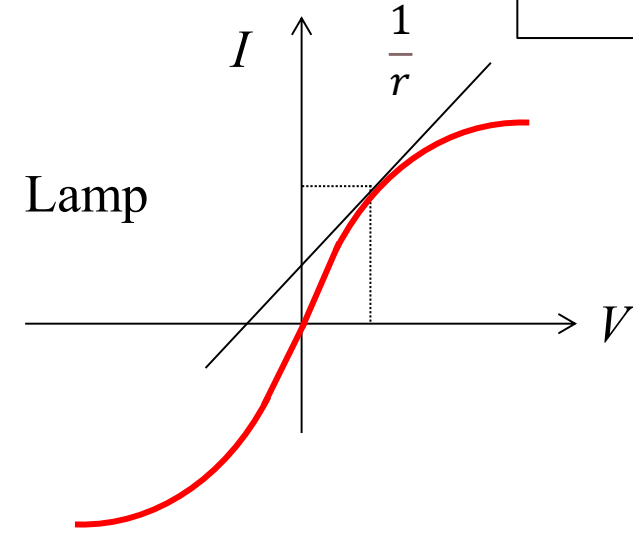

Electrical potential in a series circuit

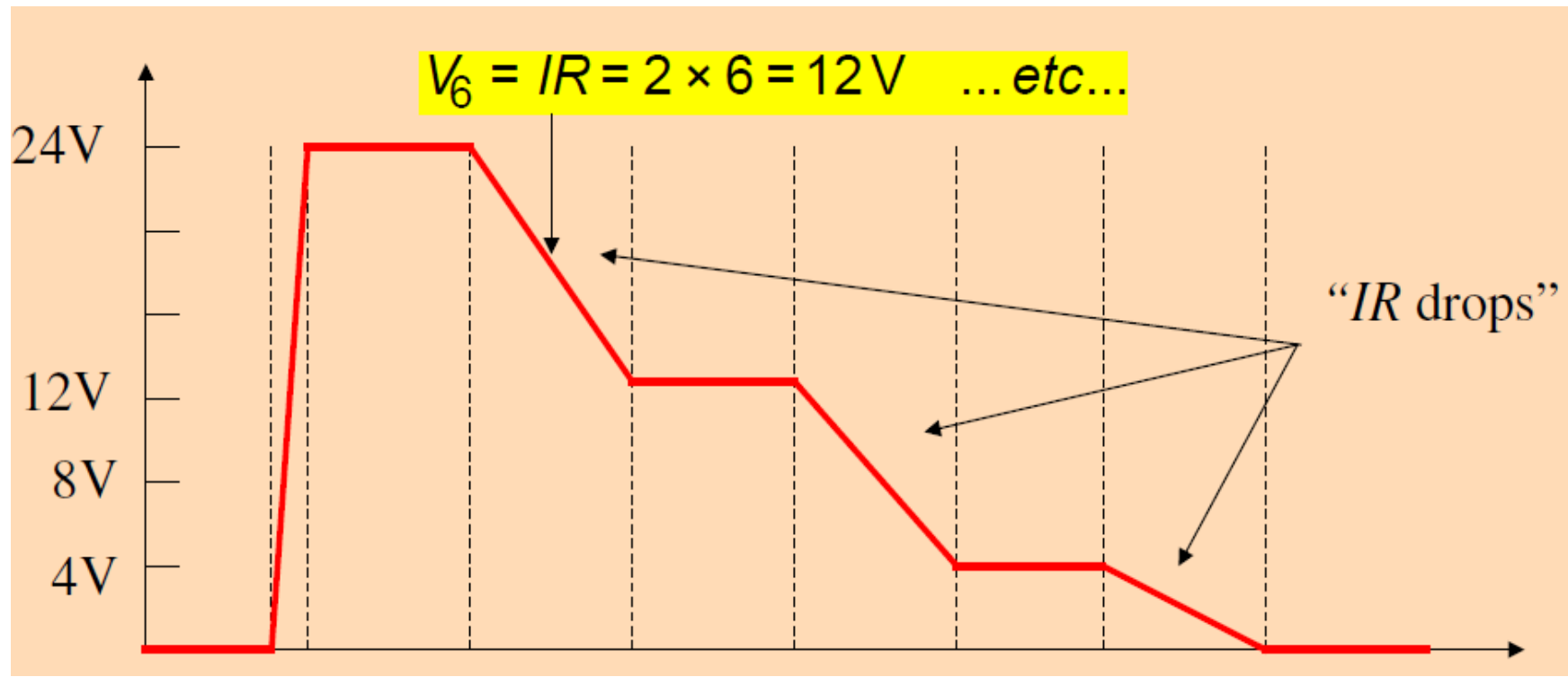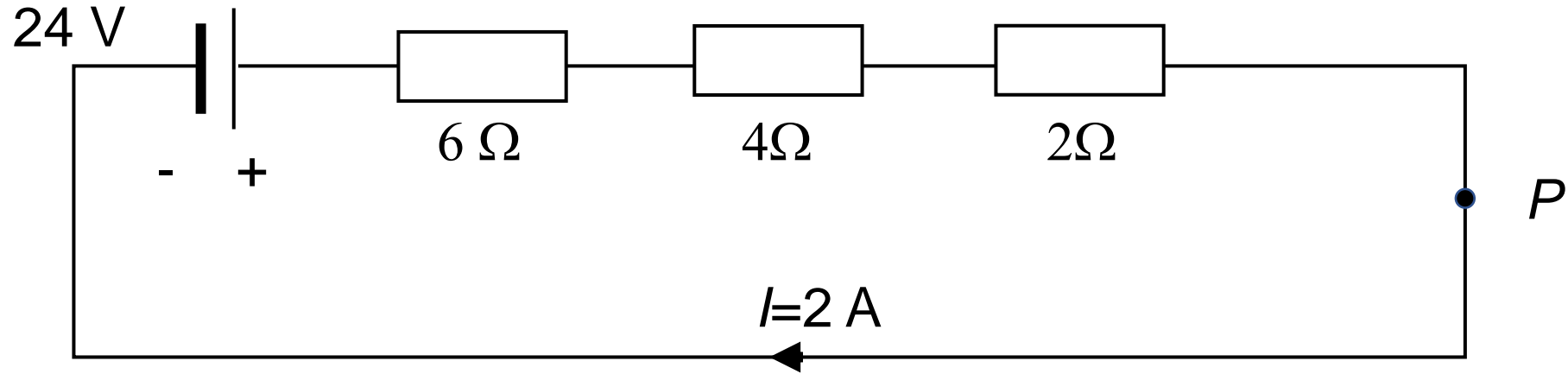


Resistors in series

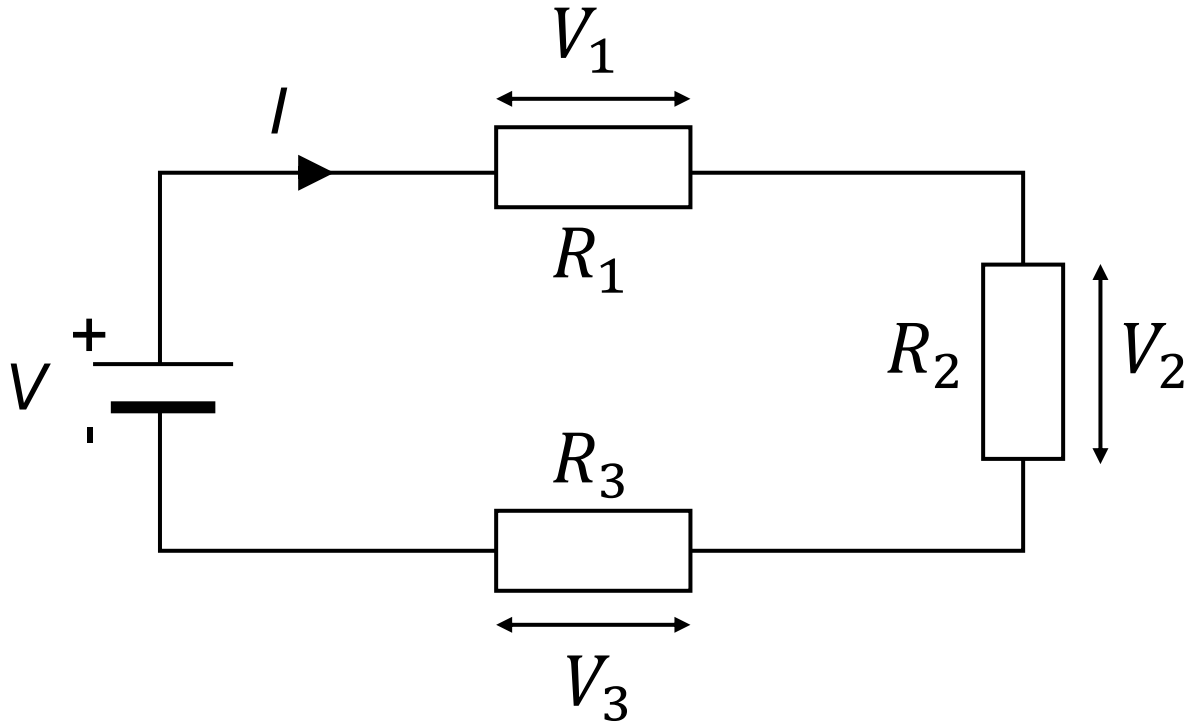

- 1) **Energy** is conserved: $V = V_1 + V_2 + V_3$
- 2) The **current** through each resistor is the same.

Equivalent circuit

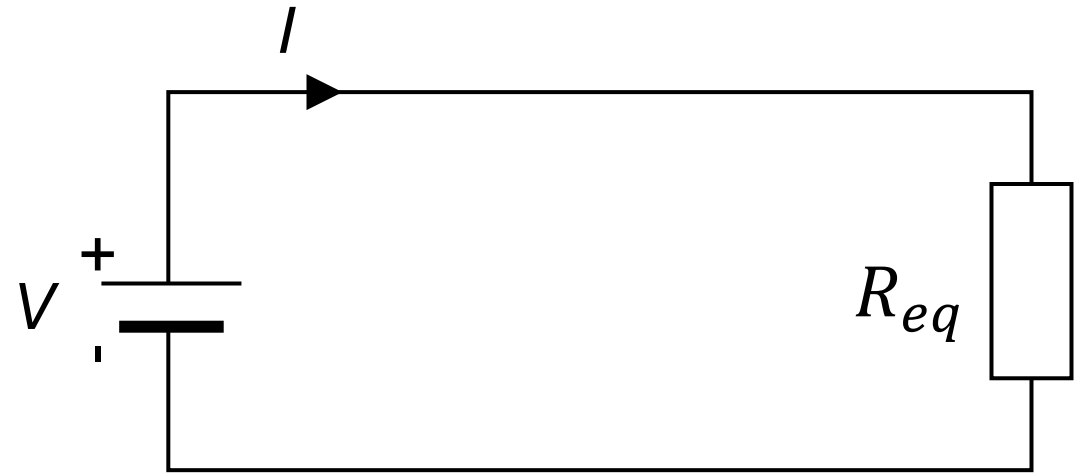


- 3) By **Ohm's law**: $V_1 = IR_1$, $V_2 = IR_2$, ...

- 4) Substituting 3) into 1):


$$V = I(R_1 + R_2 + R_3) = IR_{eq}$$

$$R_{eq} = R_1 + R_2 + R_3$$

Resistors in parallel

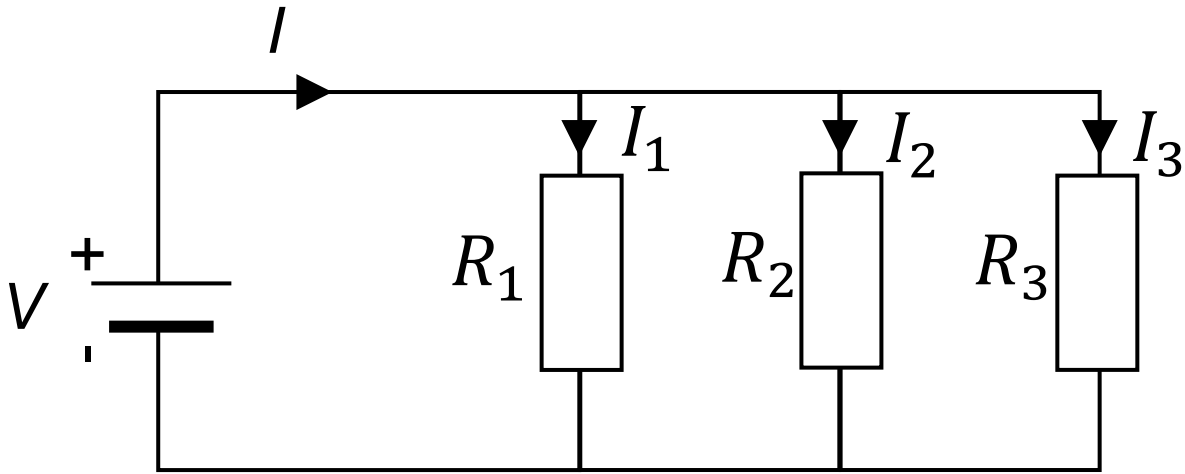

Equivalent circuit

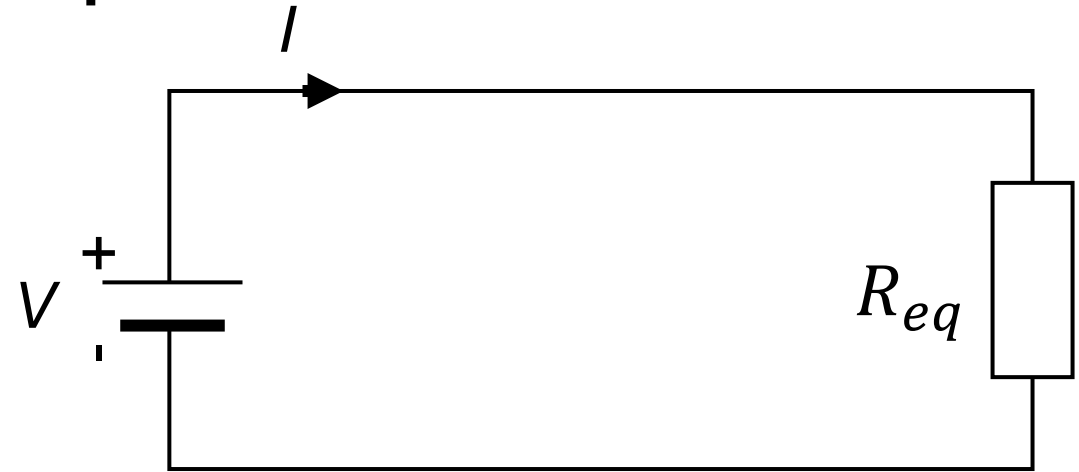

- 1) **Charge** is conserved: $I = I_1 + I_2 + I_3$
- 2) The **voltage** across each resistor is the same.
- 3) By **Ohm's law**: $I_1 = \frac{V}{R_1}$, $I_2 = \frac{V}{R_2}$, ...

- 4) Substituting 3) into 1):


$$I = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) = \frac{V}{R_{eq}}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

Two important circuit topologies


Voltage divider

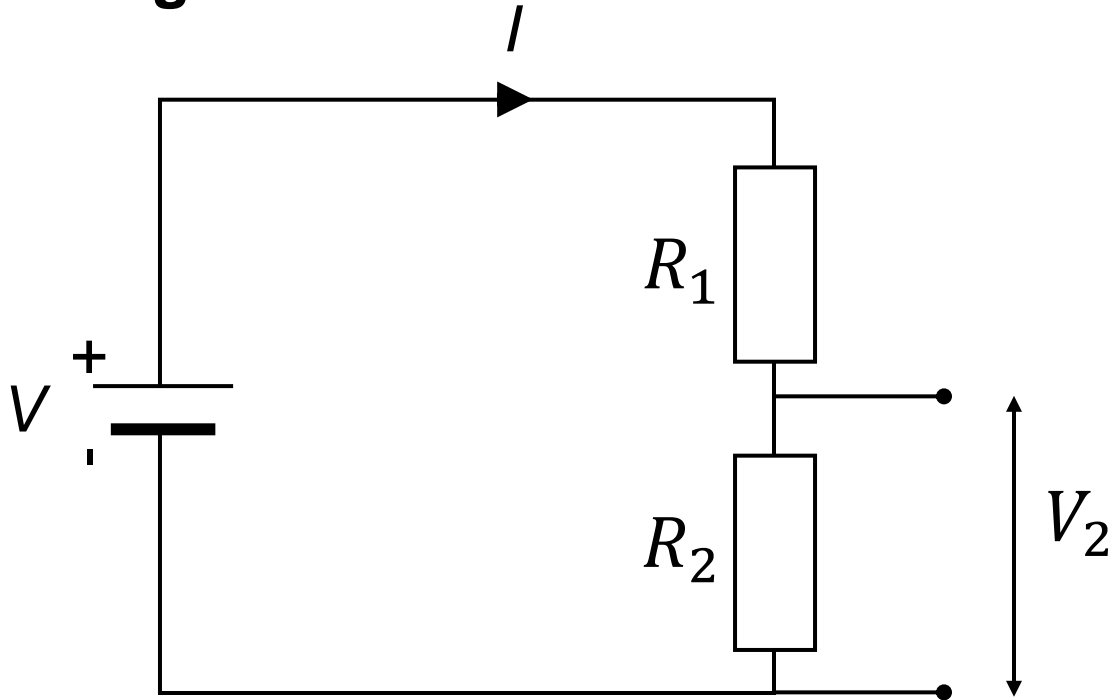

$$I = \frac{V}{R_{eq}} = \frac{V}{R_1 + R_2} = \frac{V_2}{R_2} = \frac{V_1}{R_1}$$

$$V_2 = V \frac{R_2}{R_1 + R_2}$$

Current splitter

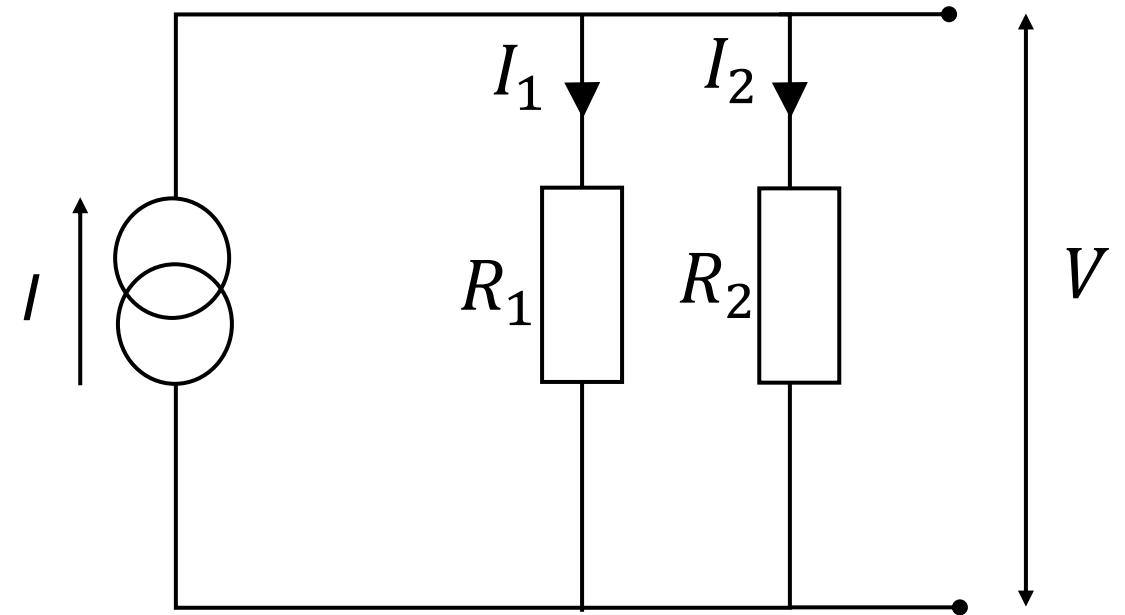

$$V = IR_{eq} = I \frac{R_1 R_2}{R_1 + R_2} = I_2 R_2 = I_1 R_1$$

$$I_2 = I \frac{R_1}{R_1 + R_2}$$

Practical applications

Electronic equipment is used every day at home and work.

What fuse would you use for:

a) a typical electric lamp?	3A	5A	13A	60A
b) a 2 kW electric kettle?	3A	5A	13A	60A
c) an electric cooker?	3A	5A	13A	60A

Where do we start?

Starting point

Ohm's law $V = IR$

What is V? V is a **potential** i.e. **potential energy** per unit charge

$$V = \frac{E}{q}$$

Energy $E = qV$

Power $P = \frac{dE}{dt} = V \frac{dq}{dt} = VI$

assuming constant V (DC)

$$P = VI = RI^2$$

Practical applications

What fuse would you use for:

- a) a typical electric lamp?
- b) a 2 kW electric kettle?
- c) an electric cooker?

3A 5A 13A 60A

3A 5A 13A 60A

3A 5A 13A 60A

Where do we start?

$$V = IR \quad P = IV$$

a) Lamp 10-20W/240V \approx 0.04-0.08 A

b) Kettle 3000W/240V \approx 12 A

c) Cooker 12000W/240V \approx 48 A

3A	5A	13A	60A
3A	5A	13A	60A
3A	5A	13A	60A

*Some fuses designed to blow if current exceeds limit for short time
others designed to survive current spikes.*

Week 01: summary

Units and definitions: current, voltage, power

Resistance, Ohm's law

Dimensional analysis

Resistors in series and in parallel

Voltage divider and current splitter

Practical applications

*Further reading: Tipler, 26-1 to 26-4
Powell, Chapters 1 and 2*

