

Year 1 Assessed Problems

Semester 2

Assessed Problems 8


SOLUTIONS TO BE SUBMITTED  
ON CANVAS BY

**Wednesday 19<sup>th</sup> March 2025  
at 17:00**

# Electric Circuits
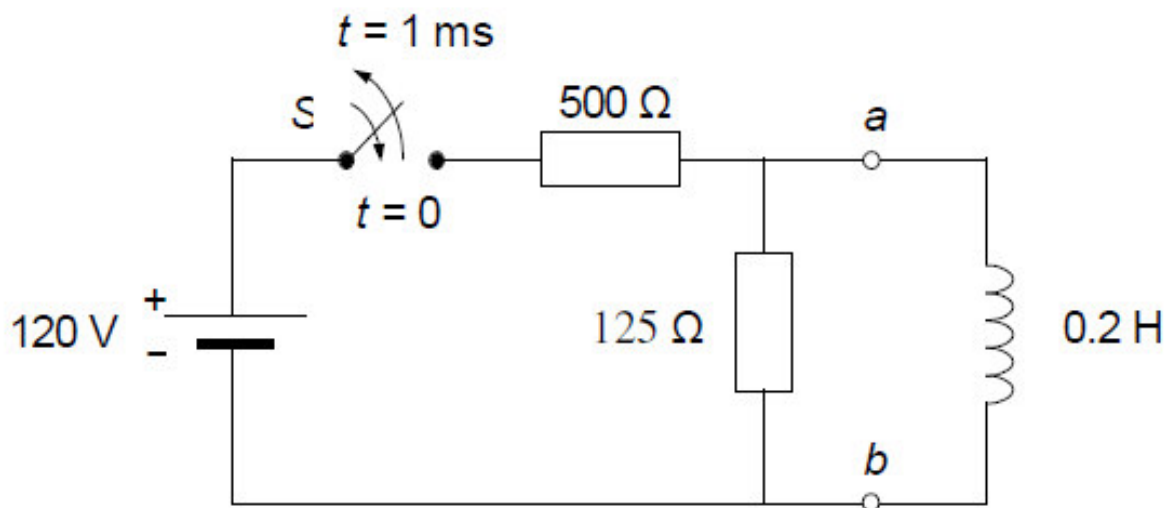
## Assessed Problem 4

After being open for a long time, the switch,  $S$ , in the circuit shown below is closed at  $t = 0$  for 1 ms, and then opened again.



Quiz Question 1:

What is the behavior of the inductor immediately after the switch is closed at  $t = 0$ ?

[1]

Quiz Question 2:

What is the initial voltage across the  $125\ \Omega$  resistor immediately after the switch is closed ( $0 < t < 1\text{ ms}$ )?

[1]

Quiz Question 3:

After a sufficiently long time after the switch has been closed, how does the inductor behave?

[1]

Quiz Question 4:

After a sufficiently long time after the switch is closed, what will be the voltage across the  $125\ \Omega$  resistor?

[1]

Continues on next page

Quiz Question 5:

While the switch is closed, what is the Thévenin equivalent resistance looking back into the circuit from the inductor's perspective?

[1]

Quiz Question 6:

What is the time constant of the circuit when  $0 < t < 1 \text{ ms}$ ?

[1]

Quiz Question 7:

What is the voltage across the  $125 \Omega$  resistor at  $t = 1 \text{ ms}$ ?

[1]

Quiz Question 8:

What is the current flowing through the inductor at  $t = 1 \text{ ms}$ ?

[1]

Quiz Question 9:

What is the voltage across the  $125 \Omega$  resistor immediately after the switch is opened ( $t > 1 \text{ ms}$ )?

[1]

Quiz Question 10:

What is the time constant of the circuit after the switch is opened ( $t > 1 \text{ ms}$ )?

[1]

## Continuous Assessment IV

Continuous Assessment for Chaos is centred around two analogue exam questions which can be found on canvas.

Consider the non-linear mapping

$$x_{n+1} = \frac{ax_n}{1 - x_n^2}$$

where  $a$  is a control parameter.

7. Find all the 2-cycles and establish when they are stable. [5]
8. Find the algebraic relationship between  $\tan \pi y$  and  $\tan \frac{\pi y}{2}$ . [5]

## Maths for Physicists 1B Assessed Problem 4

Evaluate the following indefinite integrals providing full working (2 marks each).

(a)  $\int \sin(\sqrt{x}) \, dx;$

(b)  $\int \frac{dx}{a^2 \cos^2 x + b^2 \sin^2 x}$  where  $a > 0, b > 0;$

(c)  $\int \frac{1 - \tan x}{1 + \tan x} \, dx;$

(d)  $\int \frac{dx}{\sqrt{1 + \sqrt{x}}};$

(e)  $\int \frac{dx}{\cos x + \sin x}.$