
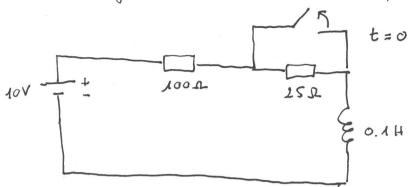
EXAMPLE 1:

Find voltage access the inductor after the switch opens.




with closed switch the circuit is:

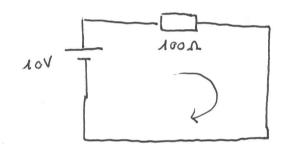

$$\begin{bmatrix} V_L = 0 \\ i = iL = \frac{V}{R_A} = \frac{10V}{100 \Omega} = 0.1 A \end{bmatrix}$$

- is short-circuited wither closed switch
- 2) the long-time response of the inducta in that of a S/c

the circuit now is:

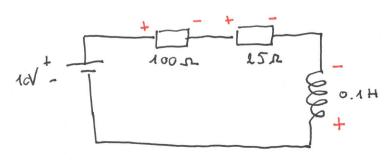

We would need to find: Vin, Vfin, ~

Vin The auruent through an inducta commot change istantoneously so $i \equiv i_L = 0.1 \, \text{A}$ (calculated above)

Uning KVL: 10V - i. 1000 - i. 250 (+)VL = 0

the induced e.m.f.
opposes to the change

L>. Rincreases

· aurent

olecreases

Vi "helps" the wrint supply to maintain the higher current.

So: VL = Vim = O.1A. (12512) - 10V = 2.5V

Vfm in the steady state the inducta will behave again as a SIC


Vfin = OV

Finally: $V_{L}(t) = 0V + (2.5V - 0V) e^{-\frac{t}{0.1 + t}}$ = 2.5V e 0.8 ms

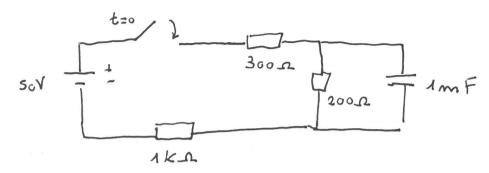EXAMPLE 2 :

In the circuit below the switch has been open for a long time, so C is fully discharged.

At t=0 the switch is closed for 10 ms and then opened again.



What is V across the 2001 resistance for t > 10 ms? Note that $V_{2001} \equiv V_c$

. t < 0


Circuit open far lag time, I fully discharged.

05t < 10ms

Vin the voltage across a capacita commot change istanta neously $Vin = 0 \vee$

Vfm with circuit closed for long time, capacitor behaves like an 0/c


So we have :

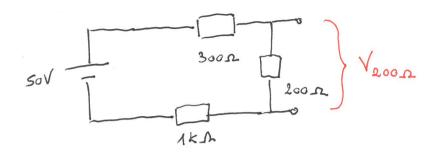

$$i = \frac{50 \text{ V}}{(300 + 200 + 1000)} = \frac{50 \text{ V}}{1500 \Omega} = \frac{1}{30} A$$

$$V_{200\Omega} = V_{c} = \frac{1}{30} A \cdot 200 \Omega = \frac{20}{3} A \Lambda = 6.67 V$$

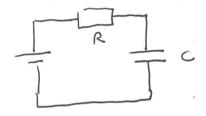We are looking for something which is like




So we have to calculate

The R (equivalent) using

procedure used for Thevenin

where R is the equivalent of Y=RC

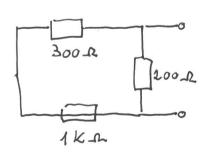

$$\frac{1}{R} = \frac{1}{1300 \Omega} + \frac{1}{200 \Omega}$$
, $R = 173 \Omega$

V= 1mF. 173 1 = 173 ms >> 10ms

in 10ms the system has not reached the steady state


$$V_{200.0}$$
 (t= 10ms) = V_c (t = 10ms)
= 6.67 (1-e - $\frac{10ms}{173mrs}$) V_c

t 3,10ms

V across the capacitor won't change abruptly

Vin Vin = 0.38V

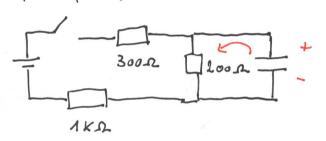Vfin after opening the switch the circuit will be



branch of the circuits forms a closed loop.

For lay times after opining the switch, C will be fully discharged. -> Vfin = OV

The state of the