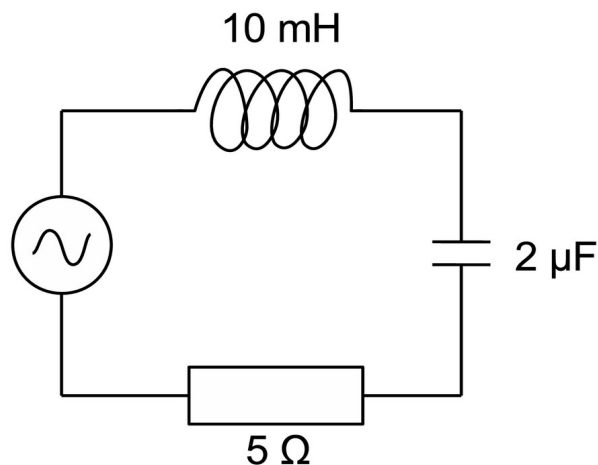


Non-assessed Week11 solution

1. Worked problem from Lecture 9.

A series LCR circuit with $L = 10 \text{ mH}$, $C = 2 \text{ }\mu\text{F}$ and $R = 5 \text{ }\Omega$ is driven by a generator with an amplitude of 100 V and variable angular frequency ω . Find **(a)** the resonant frequency ω_0 and **(b)** the rms current at resonance. When ω is 8000 rad/s find **(c)** the impedance Z , **(d)** the rms current.



The resonance condition is found by requiring the generator voltage to be in phase with the current. This occurs when the inductor reactance equals the capacitor reactance.

$$\textbf{(a)} \quad \omega_0 L = \frac{1}{\omega_0 C} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} = 7071 \text{ rad/s.}$$

At resonance the impedance is purely resistive, $Z = R$. The current magnitude and rms current are given by

$$\textbf{(b)} \quad I = \frac{V}{R} = \frac{100}{5} = 20 \text{ A} \Rightarrow I_{rms} = \frac{I}{\sqrt{2}} = 14.142 \text{ A.}$$

(c) To calculate the impedance, sum the imaginary parts for L and C and the real part from R ,

$$Z = R + j\left(\omega L - \frac{1}{\omega C}\right) = R + j\left(\frac{\omega^2 LC - 1}{\omega C}\right)$$

The magnitude of the impedance is thus,

$$Z = \sqrt{R^2 + \left(\frac{\omega^2 LC - 1}{\omega C}\right)^2} = 18.2 \text{ }\Omega.$$

The impedance is defined as the ratio of the voltage magnitude to the current magnitude ($Z = V/I$). This is just the expression of Ohm's law in a.c. circuits. Hence the rms current at this frequency is

$$\textbf{(d)} \quad I_{rms} = \frac{1}{\sqrt{2}} \times \frac{V}{Z} = \frac{100}{\sqrt{2} \cdot 18.2} = 3.885 \text{ A.}$$