

Electric Circuits

Dr Vera Guarrera

v.guarrera@bham.ac.uk

Summary of Lecture 1 and 2

1. Define charge, current, voltage, resistance and power

2. Combine resistors in series and parallel

$$R_{series} = R_1 + R_2 + R_3 + \dots \qquad \frac{1}{R_{parallel}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

3. Use dimensional analysis to verify the consistency of equations involving these quantities

4. Use the voltage divider and current splitter to analyse simple circuits

$$V_2 = V \frac{R_2}{R_1 + R_2}, I_2 = I \frac{R_1}{R_1 + R_2}$$

5. State Kirchhoff's laws and apply them to construct a set of simultaneous equations to find the unknown current in a circuit.

Lecture 3

- **Aims and Objectives**

In this lecture we will be looking at source characteristics and the consequences of internal resistance.

- **Material covered**


Ideal source characteristics.

Real (practical) source characteristics.

Maximum power transfer theorem.



Thévenin's theorem.

Thévenin's procedure and examples.

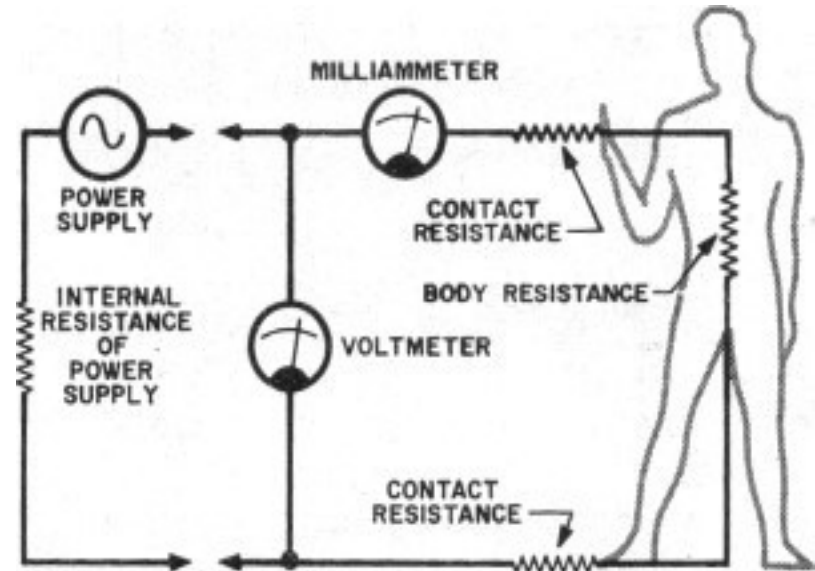

The I-V characteristics of ideal sources


IDEAL VOLTAGE SOURCE

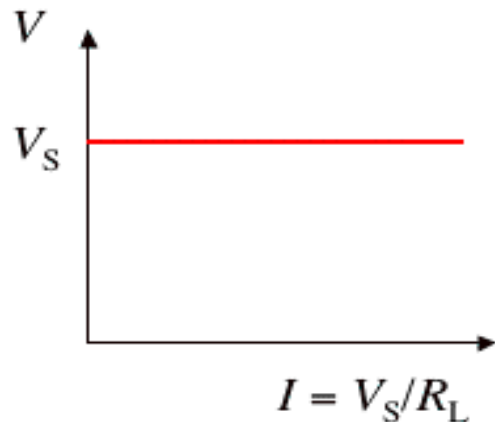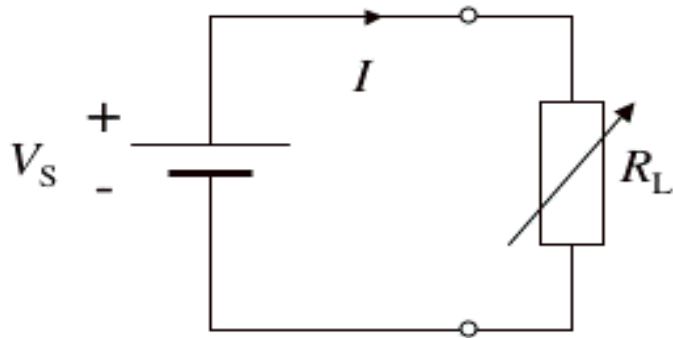


- Constant potential difference.
- The current drawn from the voltage source depends on the load resistance.

The I-V characteristics of ideal sources

IDEAL CURRENT SOURCE

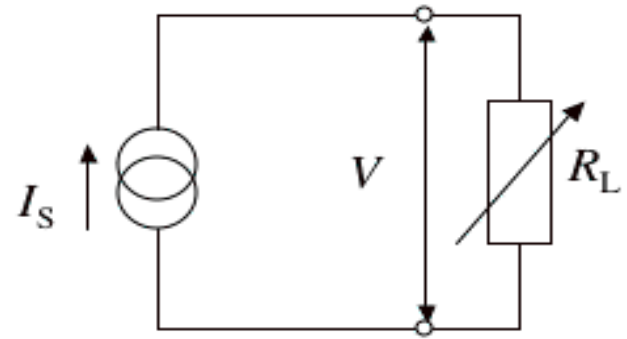

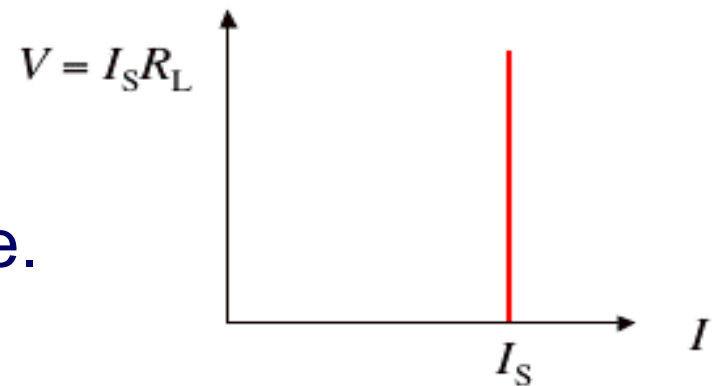
- Constant current.
- The potential difference across the current source depends on the load resistance.



What happens if...

Constant voltage

$$R_L = 0 ?$$
$$I = ?$$

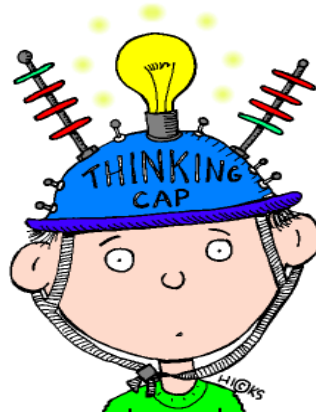

Infinite energy!

$$\text{No } I = \infty !!!$$
$$\text{No } V = \infty !!!$$

Constant current



$$R_L = \infty ?$$
$$V = ?$$





Real sources have internal resistance

Real (practical) source characteristics

• Practical voltage source

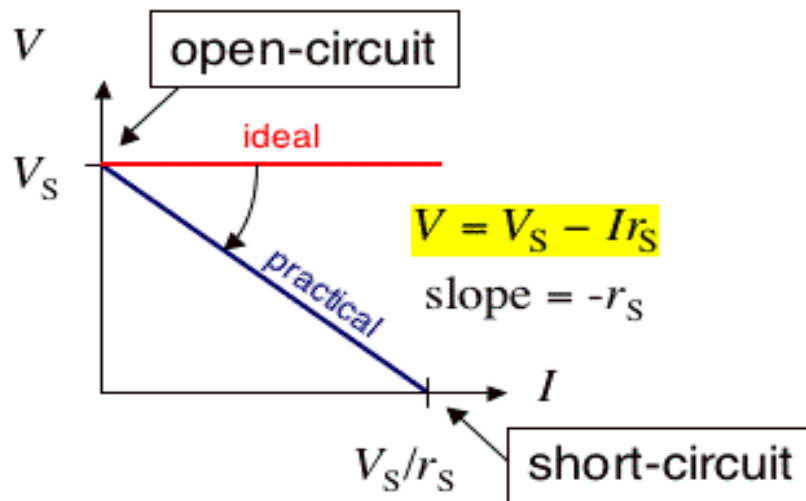
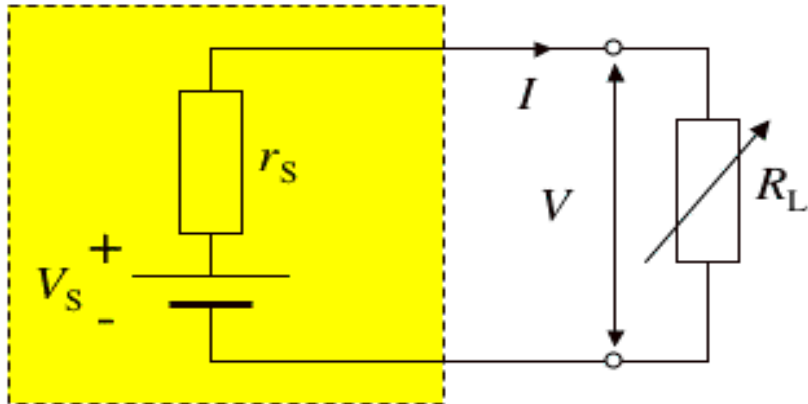


• Practical current source

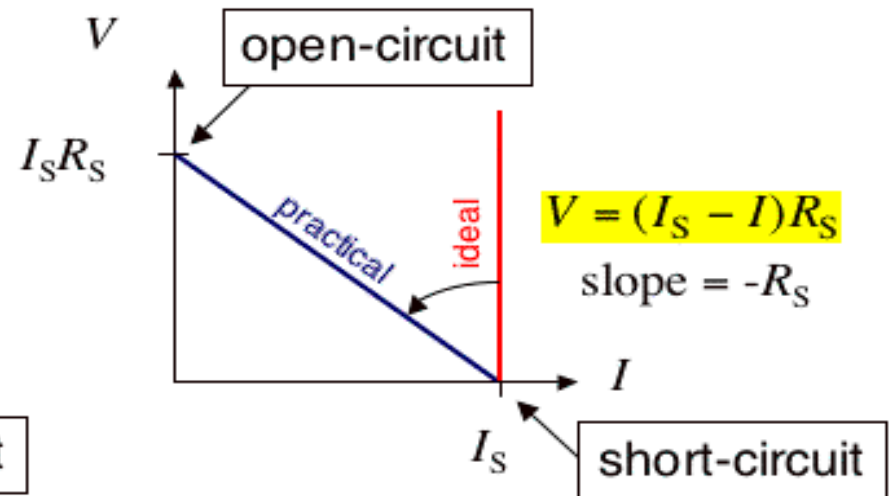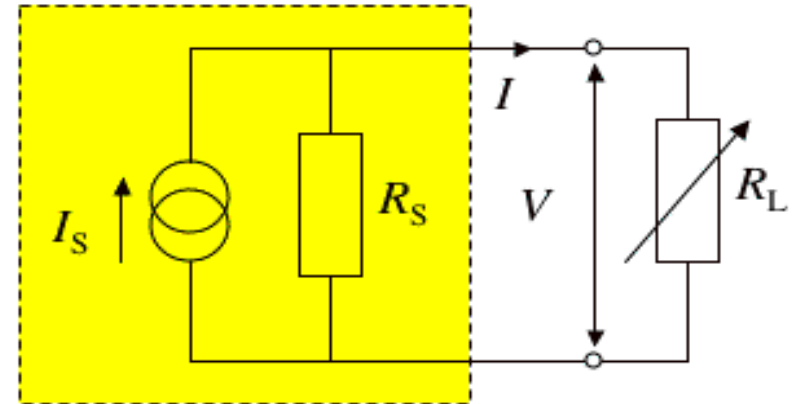

Maximum power transfer theorem

- Practical voltage source

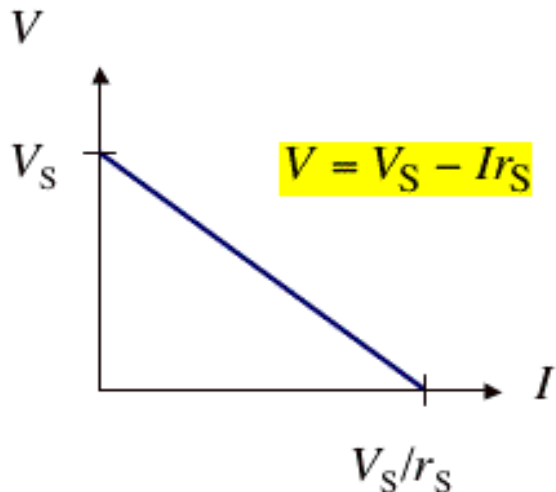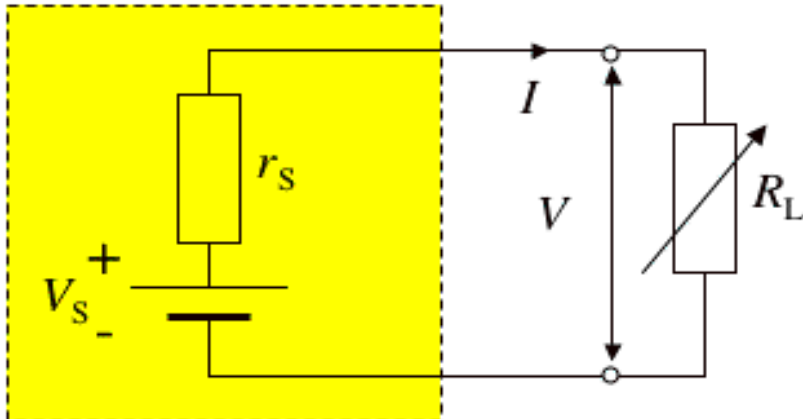

- Power in the load

$$P_L = I^2 R_L = \left(\frac{V_S}{r_S + R_L} \right)^2 R_L$$

$$\text{For max or min } \frac{dP_L}{dR_L} = 0$$

Result $R_L = r_S$, For the detailed calculation see
03_Lecture_Notes on Canvas

- Power transfer efficiency


$$\eta = \frac{P_L}{P_{\text{TOT}}} = \frac{I^2 R_L}{I^2 (r_S + R_L)}$$

$$\eta = \frac{R_L}{(r_S + R_L)}$$


$P_L^{\text{MAX}}(R_L = r_S) \rightarrow$ “impedance matching”

Power transfer and power transfer efficiency

• Power transfer

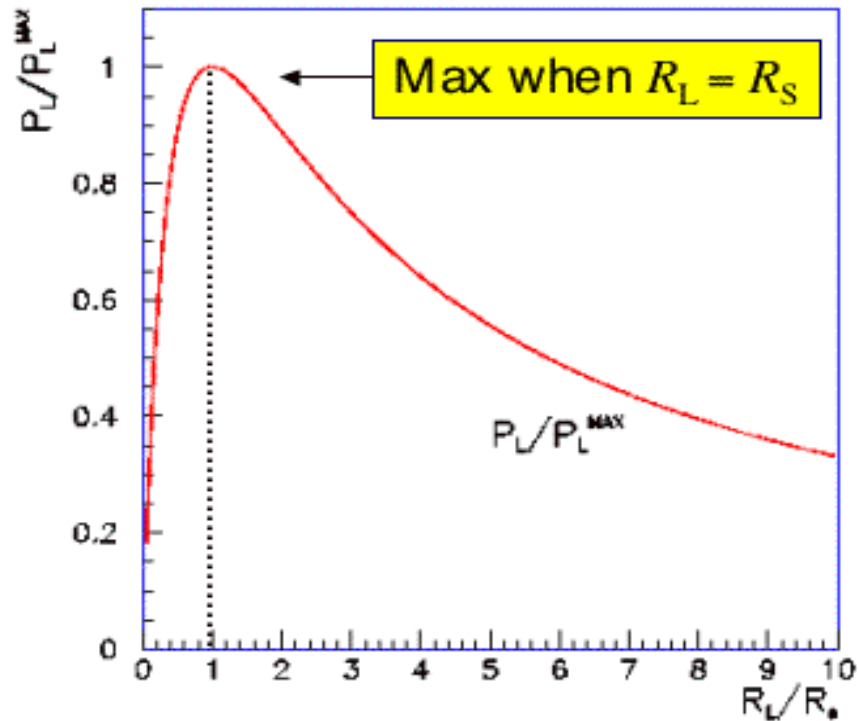

• Transfer efficiency (η)

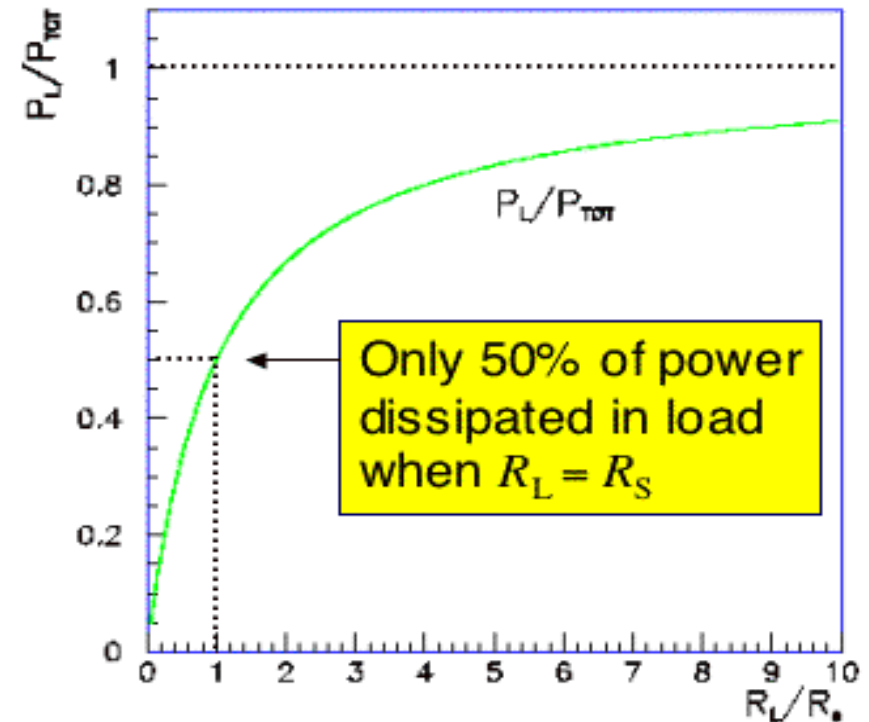


Maximum power is delivered to the load when $R_L = R_s$.

But, only 50% of the power delivered by the battery is dissipated in the load.

Equivalent circuits

- **Thévenin's theorem**

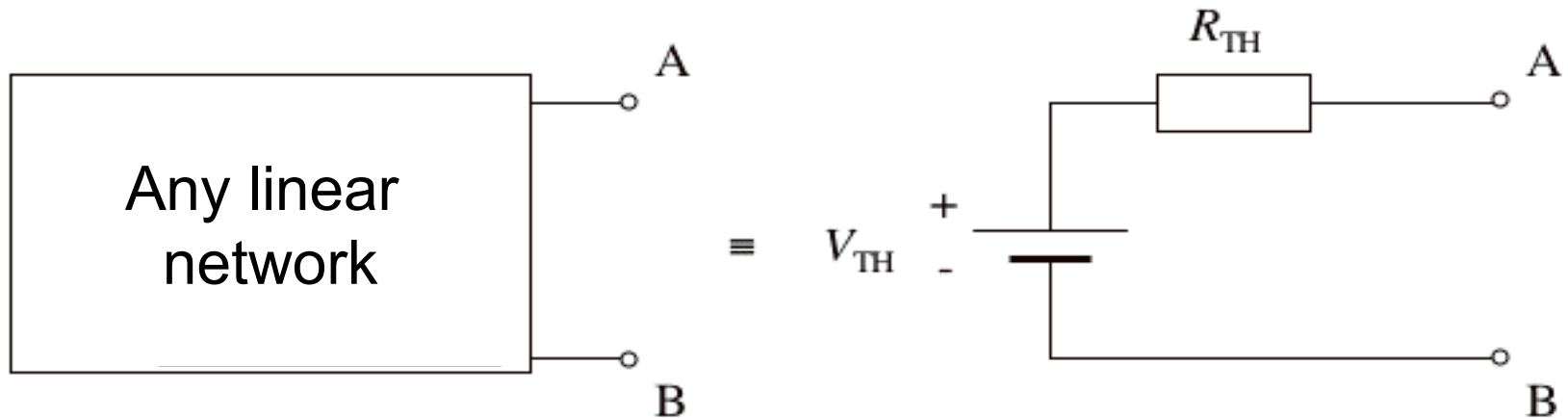Any linear network of voltage and current sources and resistors with output terminals, can be replaced at those terminals by a single voltage generator in series with a single resistor (i.e. **a practical voltage source**).



V_{TH} is the open circuit voltage between the terminals A and B.


R_{TH} is the resistance looking back into the terminals A and B.

when all generators are removed.


(Voltage generators \rightarrow s/c, Current generators \rightarrow o/c)

Removing sources


- Ideal voltage source

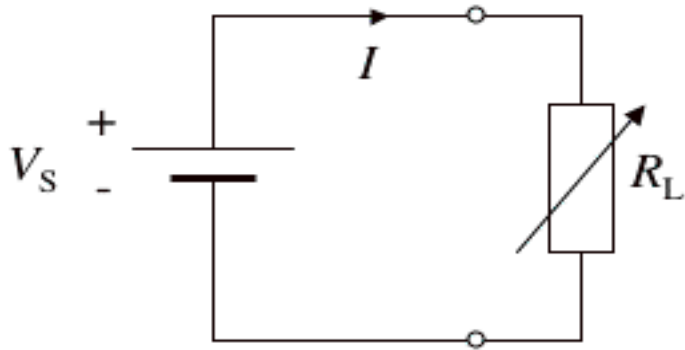


V_S constant for any load

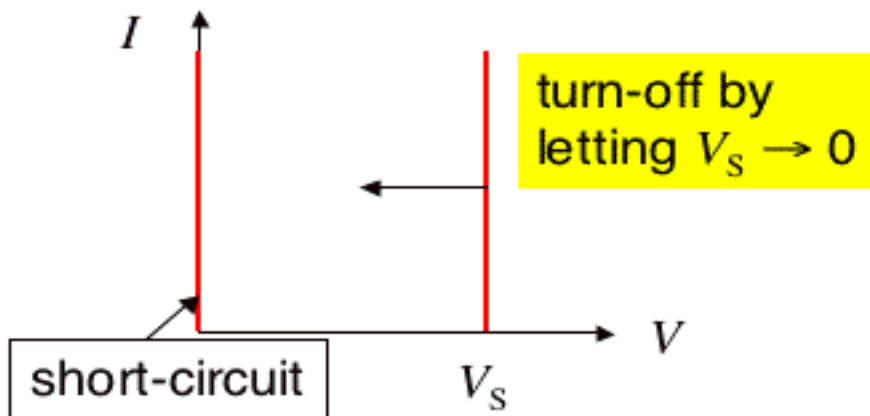

- Ideal current source

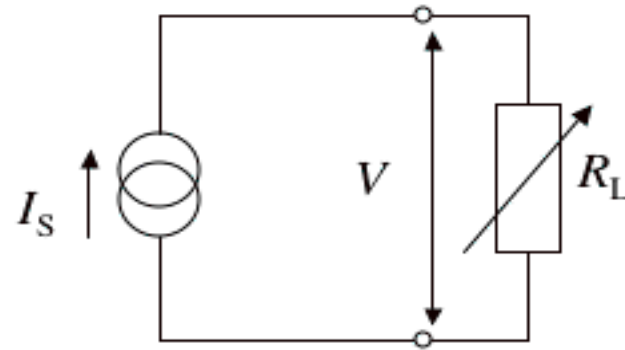

I_S constant for any load

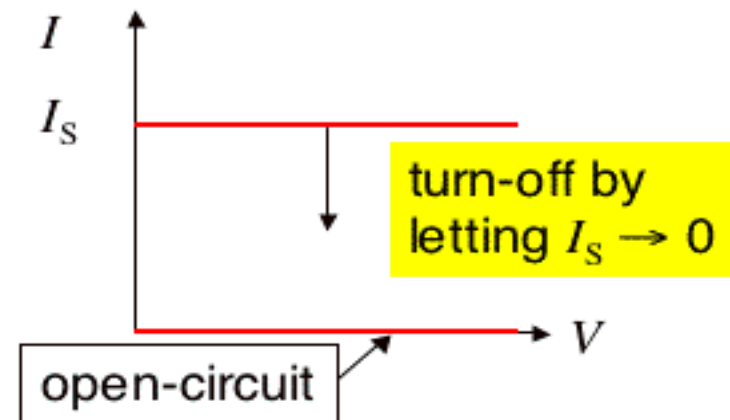

Thévenin's procedure example


- Use Thévenin's theorem to find the current in the variable load and the maximum power that can be transferred.

Method: 1. Remove the load resistor, R_L .

2. Find the Thévenin equivalent of the remaining circuit.

3. Replace the load resistor.

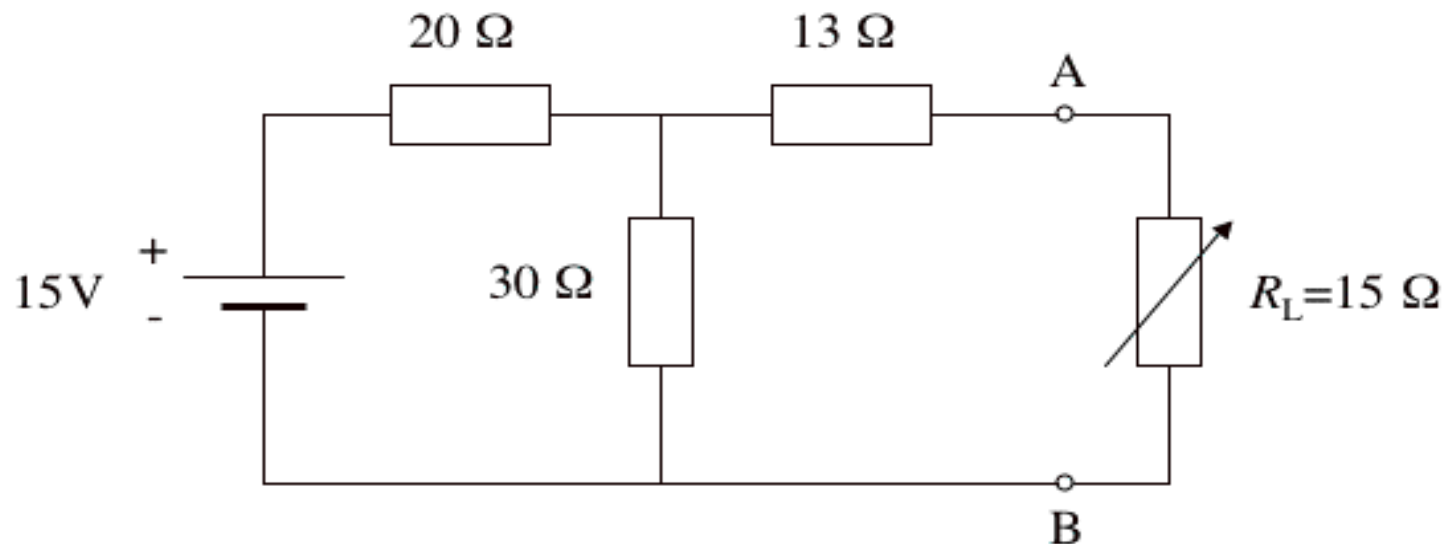4. Maximum power is transferred when $R_L = R_{TH}$.




Answer: $I = 0.225 \text{ A}$, $P = 0.81 \text{ W}$ when $R_L = 25 \Omega$

Thévenin example 2



- Find the current in the 10Ω resistor

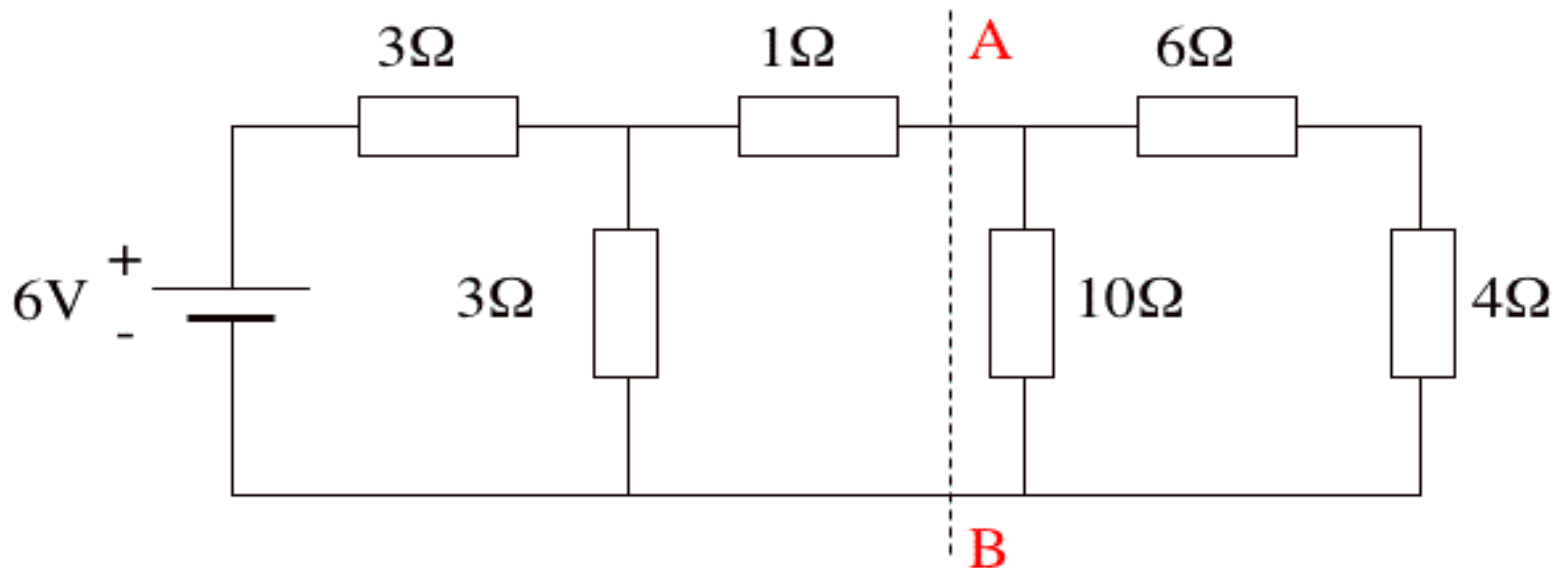- Method:
1. find the Thévenin equivalent of the circuit to the left of **AB**
 2. combine the resistances to the right of **AB**
 3. calculate the current drawn by the combined resistances
 4. use the current divider rule to find the current in the 10Ω



Answer: $V_{TH} = 3\text{ V}$, $R_{TH} = 2.5\ \Omega$, $I_{10\Omega} = 0.2\text{ A}$

Summary of Lecture 3

At the end of this lecture you should be able to:

- 1. Understand the conditions for maximum power transfer to an external circuit by a practical generator.**
- 2. Quote Thevenin's theorem and understand how to derive the Thevenin's equivalent circuit.**
- 3. Apply Thevenin's theorem in order to simplify the analysis of complex networks when only the current in part of the circuit (usually the load) is required.**

*Further reading: Powell Chapters 3.6 and 3.7
Tipler 25-3:Energy in electric circuit*