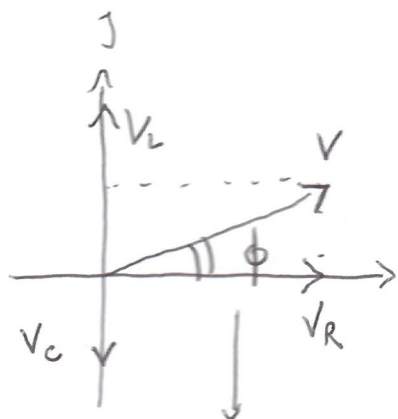


$$Z = R + j \left(\omega L - \frac{1}{\omega C} \right)$$

$$= R + j (\chi_L - \chi_C)$$

Resonance : $\text{Im}(Z) = 0$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$



ϕ = phase shift between i and v


$$V = V_L + V_C + V_R$$

$$\langle p \rangle = I_{\text{rms}} V_{\text{rms}} \cos \phi$$

$$\bullet V_L > V_C$$

$$\chi_L > \chi_C$$

~ behaves as an inductive circuit

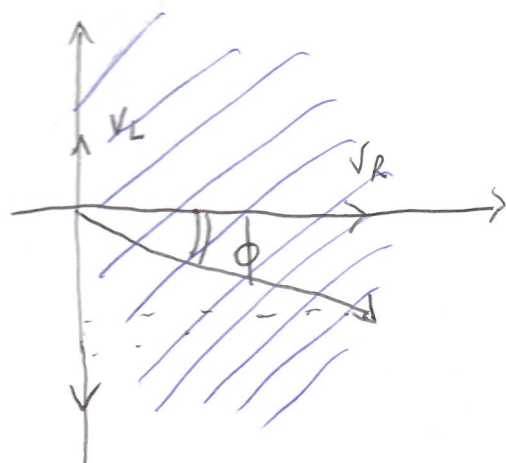

$$\bullet V_L < V_C$$


$$\chi_L < \chi_C$$

~ behaves as a capacitive circuit

$$\bullet V_L = V_C$$

$$\chi_L = \chi_C$$

Resonance

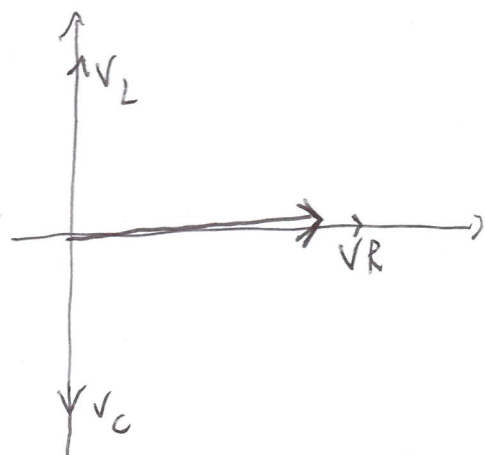

$$Q = \frac{\text{energy oscillating between L-C}}{\text{energy dissipated at R}} = \frac{X_L}{R} = \frac{\omega_0 L}{R} \equiv \frac{X_C}{R} = \frac{1}{\omega_0 CR}$$

RESONANCE

$$I = \frac{V}{|Z|} = \frac{V}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

↑
amplitude


$$= \frac{V}{R \sqrt{1 + \frac{L^2}{R^2} \left(\omega - \frac{1}{\omega LC}\right)^2}}$$

$$= \frac{V}{R \sqrt{1 + \frac{L^2}{R^2} \left(\omega - \frac{\omega_0^2}{\omega}\right)^2}}$$

$\omega_0 = \frac{1}{\sqrt{LC}}$

$$= \frac{V}{R \sqrt{1 + \frac{\omega_0^2 L^2}{R^2} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)^2}}$$
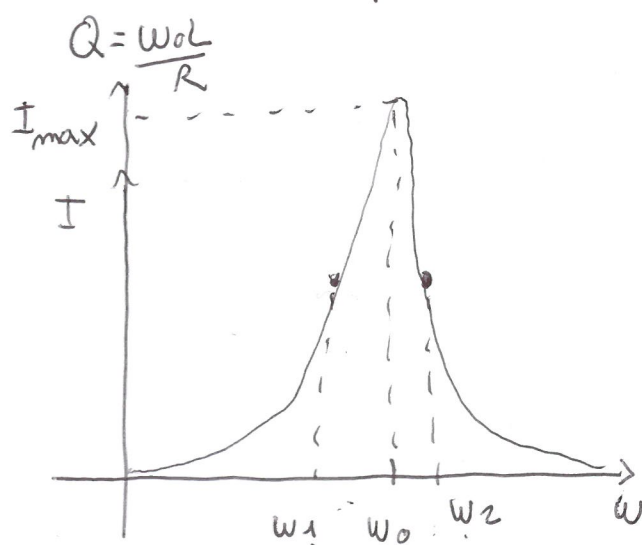
$$I = \frac{V}{R \sqrt{1 + Q^2 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)^2}}$$



$$\begin{cases} Z_{\min} \\ I_{\max} \end{cases}$$

$$= \frac{I_{\max}}{\sqrt{1 + Q^2 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)^2}}$$

$$Q^2 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)^2 = 1$$

$$I = \frac{I_{\max}}{\sqrt{2}}$$

$$Q \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right) = \pm 1$$

Solutions

$$\omega_1 \omega_2 = \omega_0^2$$

$$\omega_1 - \omega_2 = \frac{\omega_0}{Q}$$

$$\Delta \omega = \frac{\omega_0}{Q} ; Q = \frac{\omega_0}{\Delta \omega}$$