

Electric Circuits non-assessed problem Week 04

- Q3** In the circuit shown below, use the superposition theorem to find,
- the current in each resistor;
 - the potential difference between points A and B;
 - the power supplied by each battery.

